



ARTICLE

Non-Complementary Active Clamping Enables Super-Dense Flyback Power Supplies

Roland Saint Pierre | Director of New Product Definition

Off-line flyback power supplies require a clamp circuit (sometimes called a snubber) on the primary side of the transformer to limit the drain-source voltage stress on the power MOSFET when this switch turns off during normal operation. There are several approaches to designing these clamp circuits. Low-cost passive networks are effective but must dissipate the clamp energy each cycle, reducing efficiency. Active clamps employing complementary drive techniques for the clamp and power switch are an improvement and can be much more energy efficient, but they impose operating limitations on the power supply's operating modes (no CCM operation, for example). A more advanced control technique – non-complementary active clamping – ensures the most cost-effective use of clamp energy and avoids the design limitations imposed by complementary active clamp circuits.

This article briefly reviews the need for a primary clamp circuit in flyback power supplies. It then compares and contrasts the use of passive clamping with complementary and non-complementary active clamping solutions and introduces a chipset that enables the use of non-complementary clamping solutions and the design of super-dense flyback power supplies.

In a flyback converter, voltage (VOR) is reflected from secondary side when the primary side switch is turned off and the stored energy is transferred to the load through transformer (Figure 1). VOR is amplified by the transformer turns-ratio and adds to the voltage stress on the switching device imposed by the V_{DC} input rails. In conventional circuits, a passive primary clamp is added to limit this voltage excursion.

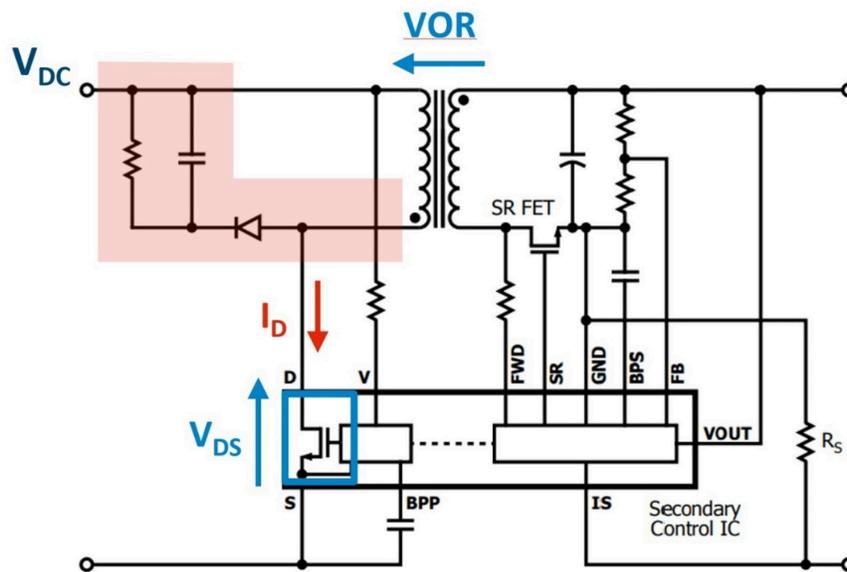


Figure 1: A passive primary clamp RCD solution (highlighted) is highly dissipative and limits the efficiency and operating frequency of flyback power supplies.

In addition to voltage stress ($V_{IN} + VOR$), there is a large voltage overshoot at turn-off caused by the stored energy in the leakage inductance of the primary winding. The clamp limits the voltage overshoot caused by these three elements and protect the primary switch (Figure 2). In addition, with this circuit configuration, the power switch turns on when the drain voltage is high. Switching loss is proportional to V_{DS}^2 , so a high V_{DS} increases turn-on losses in the switch, further decreasing efficiency.

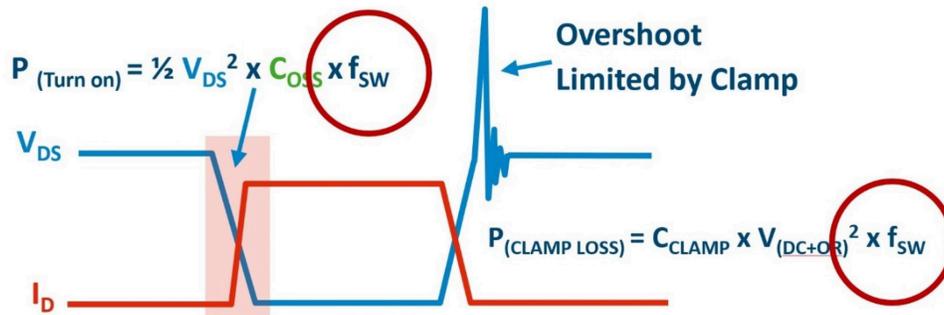


Figure 2: Turn-on losses and clamp losses are both related to switching frequency.

The clamp capacitor absorbs the leakage-inductance energy, but that energy is then dissipated by the clamp resistor. Energy is lost during every switching cycle, limiting the switching frequency in practical designs. Lower switching frequencies require larger transformers. So, the use of a passive clamp increases losses and reduces switching frequencies, both of which contribute to larger power supplies. An active clamp can be used to address those limitations.

Complementary active clamps

An active clamp replaces the resistor in an RCD clamp with a switch, usually a power MOSFET (Figure 3). Instead of dissipating the leakage inductance energy, it recycles the energy back to the transformer. In a complementary active clamp, the clamping switch is turned on when the main MOSFET is turned off, with a small amount of deadtime inserted between these events. The clamp capacitor gets charged, and just before the main MOSFET turns on, the clamp switch is turned off and the energy in the clamp capacitor is recirculated to the output. This active clamp is called a complementary drive scheme, because the main MOSFET and the active clamp switch act in a complementary fashion.

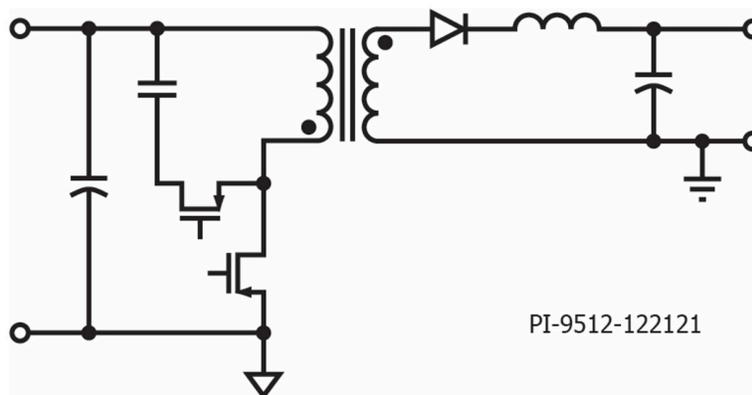


Figure 3: Simplified schematic of a typical [complementary] active clamp implementation.

Zero voltage switching can be implemented using sophisticated adaptive control techniques to achieve resonance between the leakage inductance and clamp capacitor. The leakage inductance resonates with the clamp capacitor when the clamp switch turns off in order to discharge the power MOSFET's COSS prior to turning on, resulting in zero-voltage switching. The resonant action will be rendered ineffective by a high output capacitance (reflected to the primary via transformer action adding to the clamp capacitance). There is insufficient leakage energy available in a typical transformer to accommodate this capacitance. To overcome this, a two-stage LC filter is required to both ensure a low value primary capacitance and meet output ripple requirements. This complementary active clamp solution is an improvement over a passive clamp, but still has limitations including:

1. The need to use burst mode at light load, which results in higher output ripple
2. Two-stage output filter
3. Limited to critical conduction mode or discontinuous conduction mode (CrM and DCM); no CCM operation makes wide-output USB PD designs difficult to implement

Increased performance with non-complementary active clamping

With non-complementary control, instead of turning the clamp switch on shortly after the main MOSFET is turned off, the clamp switch is turned on for a short period just before the main MOSFET turns on. Non-complementary control is able to operate in continuous conduction mode, as well as discontinuous conduction mode (and CrM), and still implement zero voltage switching. That enables the design of power supplies that have very wide input voltage ranges, as well as large output voltage ranges which are needed when designing efficient USB PD chargers. With conventional control schemes, the synchronization of the non-complementary clamp drive with primary and synchronous rectification switching can be challenging. The adoption of a single controller to manage the switching of all three devices greatly simplifies the circuit and ensures reliable operation.

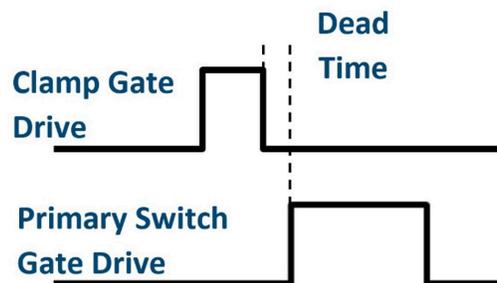


Figure 4: With non-complementary mode switching, the active clamp is cycled just before the primary switch.

Non-complementary active clamp control can be implemented using the InnoSwitch™4-CZ / ClampZero™ chipset from Power Integrations (Figure 5). InnoSwitch4-CZ devices feature a robust PowiGaN™ 750 V switch, secondary controller directing operation of the main switch, clamp switch and the synchronous MOSFET, and an internal safety-rated control link – FluxLink™, in a single InSOP™-24D package. InnoSwitch4-CZ ICs include two pins dedicated to the non-complementary control of the ClampZero active clamp; the high-side drive (HSD) pin to turn the ClampZero on and off, and the V pin for measuring the DC rail voltage.

For more information,
visit power.com[™]



© 2022 Power Integrations, the Power Integrations logo, power.com, InnoSwitch, ClampZero, PowiGaN, FluxLink and InSOP are trademarks or registered trademarks of Power Integrations, Inc., in the U.S. and/or other countries.